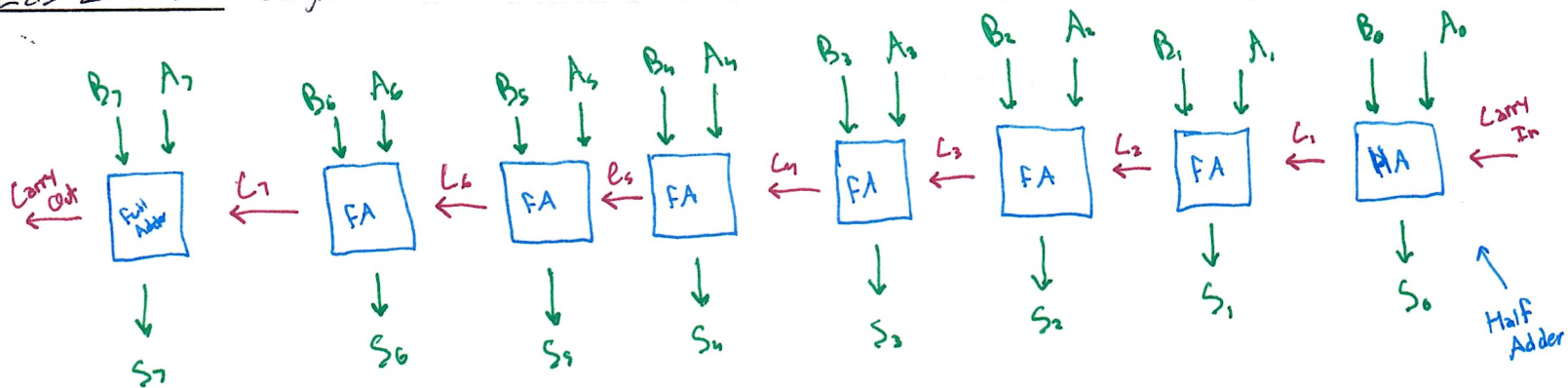


Vivian Do

CSC 3210



Lab 2 b 2c

Lab 2 b 1: design a 8-bit adder with block diagram



Lab 2 b 2: draw circuit for boolean expression: $P = (X \text{ and } Y) \text{ or } (\text{not } X \text{ or } Z)$
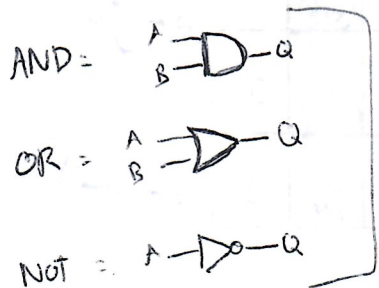 
$$P = (X \wedge Y) \vee (\neg X \vee Z)$$



Gates Needed

Lab 2 c 1 : store 12784569h in EAX register

12784569h → EAX register



4 bytes

Lab 2 c 2 : for each add instruction in this exercise, assume that EAX contains the given contents before instruction is executed

- numbers in hex
- fill out chart
- assume that numbers = signed integers

Contents of EAX (Before)	Instruction	Contents of EAX After	CF	OF	SF	ZF
00000040	add eax, 40	10000000	0	0	0 (true)	0
FFFFFF40	add eax, 40	FFFFFF80	0	0	1 (negative)	0
00000040	add eax, -40	0	0	0	0 (true)	1

(Non-zero results)

(zero result)

1) 00000040 ⇒ 01000000, 40 ⇒ 01000000
 01000000 + 01000000 = 10000000

2) FFFFFFF40 + 00000040 = FFFFFFF80

3) 00000040 - 00000040 = 0